

HW CNS1.2 - The Passive Membrane

Neuronal Dynamics – Exercises 1.2 = Homework 1.1

General Equation

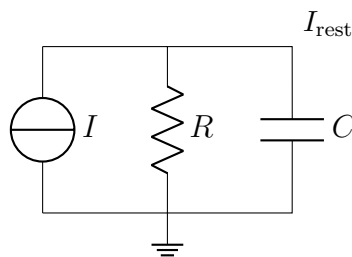


Figure 1: *
Passive membrane RC circuit

The general equation (with $V = u - u_{\text{rest}}$):

$$C \frac{du}{dt} = -(u - u_{\text{rest}}) + RI(t) \quad \Rightarrow \quad \tau \frac{dV}{dt} = -V + RI(t)$$

Case i) Step Current Input

Qualitative features

Before the timestamp of step current, voltage will remain *constant* and after it will *exponentially increase* toward RI_0 .

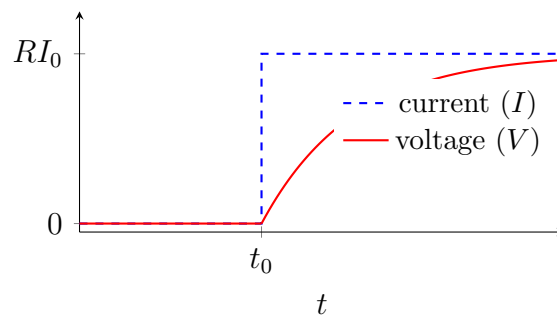


Figure 2: *
Step current (blue, dashed) and voltage response (red)

Differential Equation Derivation

i) Before step function time ($t < t_0, I = 0$):

$$\tau \frac{dV}{dt} = -V + R \underbrace{I(t)}_{=0}$$

Two sub-cases:

If $V(0) = 0$:

Equivalently:

$$\frac{dV}{V} = \frac{-dt}{\tau} \Rightarrow \ln V = \frac{-t}{\tau} \Rightarrow V = V_0 e^{-t/\tau} \quad \int \frac{dV}{V} = \int \frac{R I(i)}{\tau} dt \Rightarrow dV = 0$$

With $V(0) = 0 \Rightarrow V(t) = 0$

$\Rightarrow V$ remains constant

ii) Step current hits ($t \geq t_0, I = I_0$):

$$\tau \frac{dV}{dt} = -V + R I(t)$$

Substitute $W = V - RI_0$ (so $dV = dW$, $W_0 = V(t_0) - RI_0 = -RI_0$):

$$\begin{aligned} \tau \frac{dW}{dt} &= -W \Rightarrow \frac{dW}{-W} = \frac{dt}{\tau} \\ \Rightarrow \int_{W_0}^{W(t)} \frac{dW}{W} &= \int_{t_0}^t \frac{dt}{\tau} \Rightarrow -\ln\left(\frac{W(t)}{W_0}\right) = \frac{t - t_0}{\tau} \\ \Rightarrow W(t) &= W_0 e^{-(t-t_0)/\tau} \quad (W_0 = -RI_0) \end{aligned}$$

Back-substitute $V(t) = W(t) + RI_0$:

$$\boxed{V(t) = RI_0(1 - e^{-(t-t_0)/\tau}), \quad t \geq t_0}$$

Case ii) Pulse Current Input

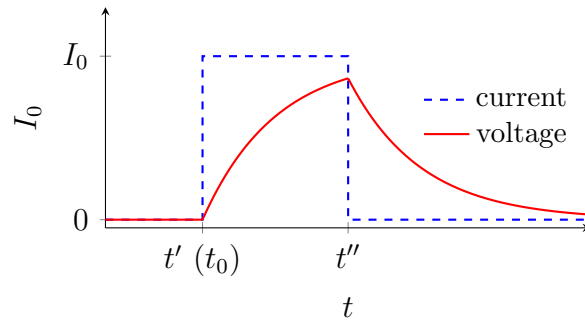


Figure 3: *

Pulse current and voltage response. Labels: $t' = t_0$, $t'' = \text{end of pulse}$, $\Delta t = t'' - t'$

Qualitative feature

The whole curve can be broken down in **3 phases**: pre-pulse stage, pulse current, and post-pulse current. First two phases are analogous to the two phases of Case i. At the end of the 3rd phase, our V is approaching RI_0 , but while approaching I_0 , current supply is cut down, so our voltage will decrease. We have to find the equation for that.

Phase 3 – After pulse ($t > t''$, $I = 0$):

$$\tau \frac{dV}{dt} = -V \quad \Rightarrow \quad \frac{dV}{V} = \frac{-dt}{\tau} \quad \Rightarrow \quad \ln\left(\frac{V(t)}{V''}\right) = -\frac{t - t''}{\tau}$$

where $V'' = V(t'')$ is the potential at the end of the pulse (depends on time interval of pulse):

$$V'' = RI_0(1 - e^{-\Delta t/\tau}), \quad \Delta t = t'' - t'$$

$$V(t) = V'' e^{-(t-t'')/\tau} = RI_0(1 - e^{-\Delta t/\tau}) e^{-(t-t'')/\tau}, \quad t > t''$$

Case iii) Arbitrary Current Output

We *can't* split into constant pieces, so we use the **integrating factor method** on the full ODE.

Step 1 – Standard linear form

$$\frac{dV}{dt} + \frac{V}{\tau} = \frac{R}{\tau} I(t) \quad \left(\text{standard: } \frac{dV}{dt} + p(t)V = q(t) \right)$$

Step 2 – Integrating factor

$$\mu(t) = e^{\int (1/\tau) dt} = e^{t/\tau}$$

Step 3 – Multiply both sides by μ

$$\begin{aligned} e^{t/\tau} \frac{dV}{dt} + e^{t/\tau} \frac{V}{\tau} &= \frac{R I(t)}{\tau} e^{t/\tau} \\ \Rightarrow \frac{d}{dt} (e^{t/\tau} V) &= \frac{R I(t)}{\tau} e^{t/\tau} \end{aligned}$$

Step 4 – Integrate both sides

$$e^{t/\tau} V(t) - V_0 = \frac{R}{\tau} \int_0^t e^{s/\tau} I(s) ds$$

Final result

$$V(t) = V_0 e^{-t/\tau} + \underbrace{\frac{R}{\tau} e^{-t/\tau} \int_0^t e^{s/\tau} I(s) ds}_{\text{accumulated input, each weighted by how long ago it arrived}}$$